

**PRACTICAL ASSIGNMENT**

**MODUL 3**

**DIGITAL SYSTEM**



**By:**

**M. RIFQY FAUZY**


**L200184090**

**INFORMATION TECHNOLOGY**

**COMMUNICATION AND INFORMATICS FACULTY**

**MUHAMMADIYAH UNIVERSITY OF SURAKARTA**

# 1. Create a logic gate combination

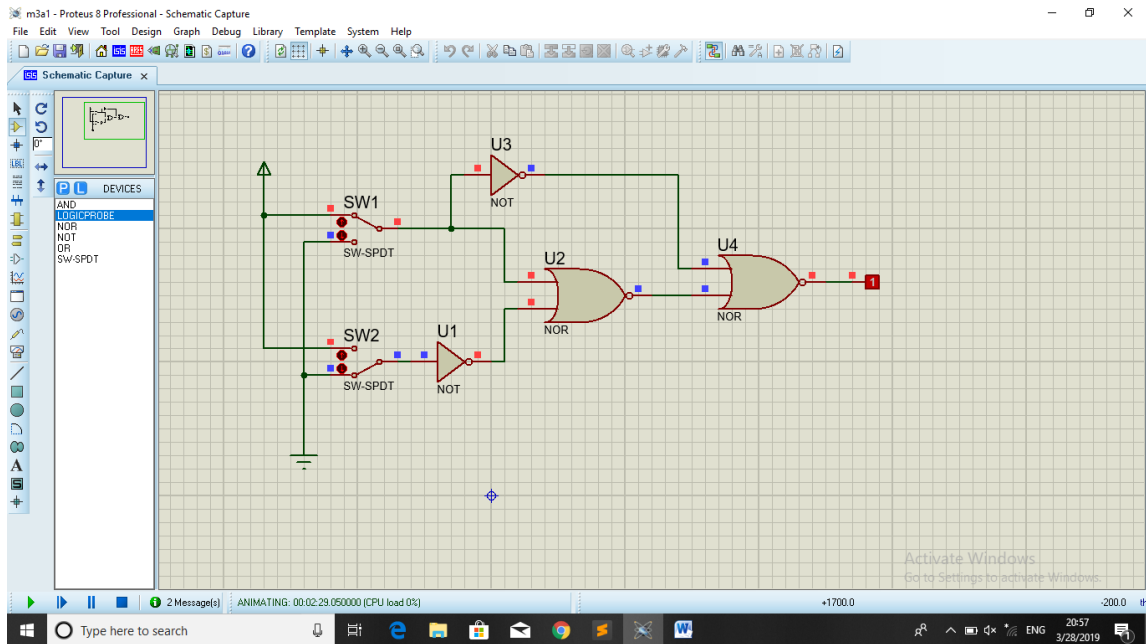


## a. Truth table and time diagram

### i. Truth table

SW1	SW2	F
0	0	0
0	1	0
1	0	1
1	1	1

### ii. Time diagram

**F**

 

## b. Boolean function

$$F = \neg(\neg X + \neg(X + Y)) = X(X + \neg Y)$$

## 2. Create a logic gate circuit based on the following Boolean function!

$$F = \neg((\neg A)B + C) + ((\neg D)E)$$

