

PRACTICAL REPORT

MODUL 3

DIGITAL SYSTEM



By:

M. RIFQY FAUZY

L200184090


INFORMATION TECHNOLOGY

COMMUNICATION AND INFORMATICS FACULTY

MUHAMMADIYAH UNIVERSITY OF SURAKARTA

1. Trial 1: Substitution for Logic Gate Substitute

1. Make the circuit.

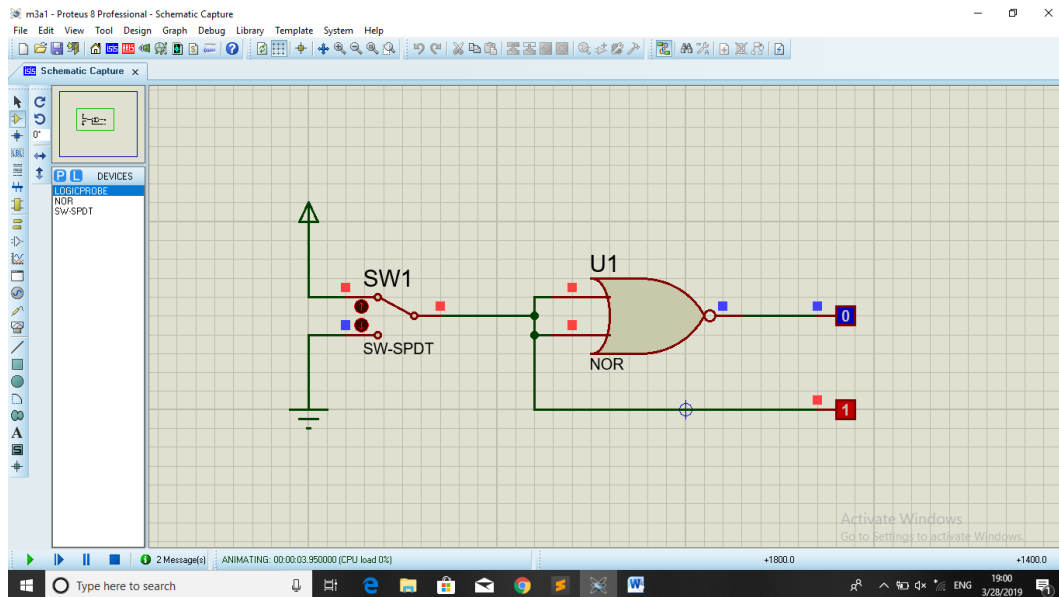


$$2. L1 = \text{NOT}(L2 + L2) = L2$$

3. Truth Table

SW1	L2	L1
0	0	1
1	1	0

4. Time Diagram

 


5. Conclusion:

NOR gate in figure 4.3 form a logic from the **NOT** gate.

2. Trial 2: Substitution for Logic Gate Substitute

1. Make the circuit.

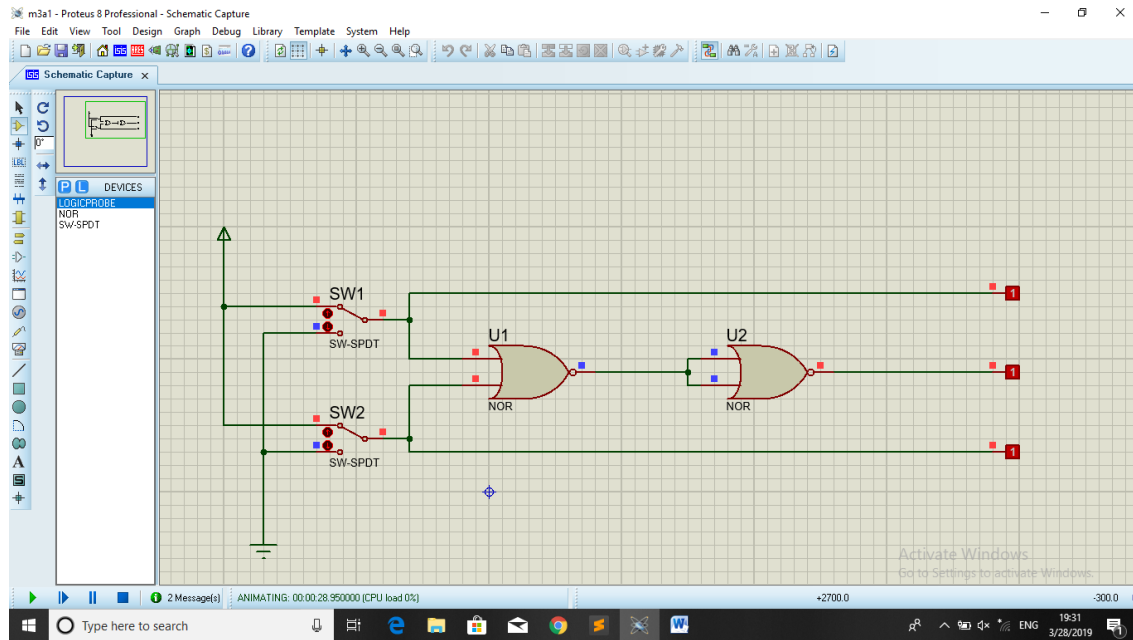


2. $L3 = \text{NOT}(\text{NOT}(L1+L2)) = L1 + L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1

4. Time Diagram

 


5. Conclusion:

The NOR gate in figure 4.4 form a logic from the **OR** gate.

3. Trial 3: Substitution for Logic Gate Substitute

1. Make the circuit

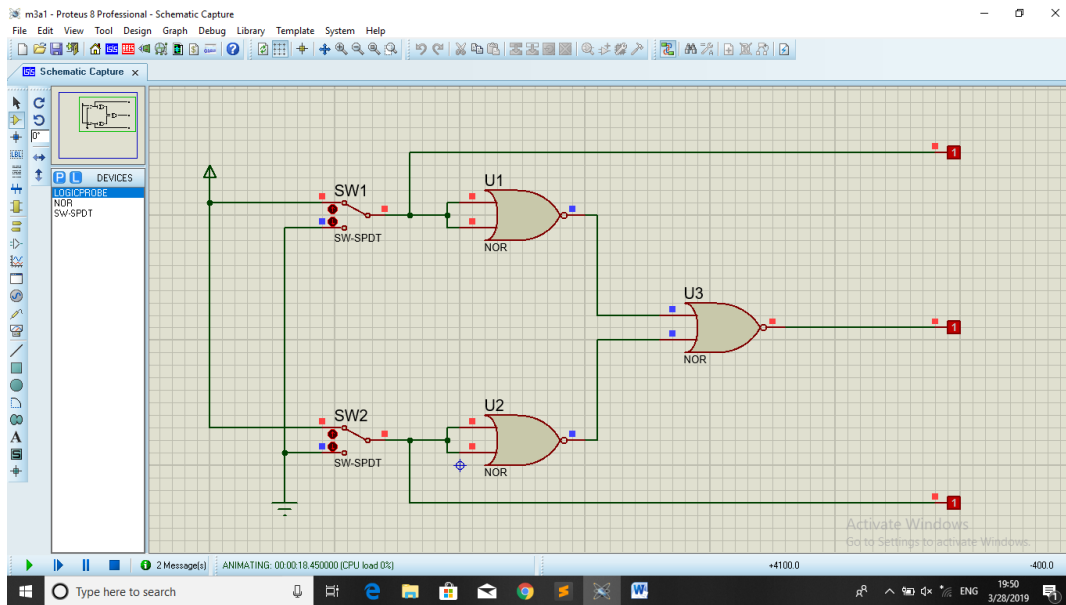


2. $L3 = \text{NOT}(\text{NOT}(L1) + \text{NOT}(L2)) = L1 L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

4. Time Diagram

 


5. Conclusion

The NOR gate in figure 4.5 form a logic from the **AND** gate.

4. Trial 4: Substitution for Logic Gate Substitute.

1. Make the circuit.

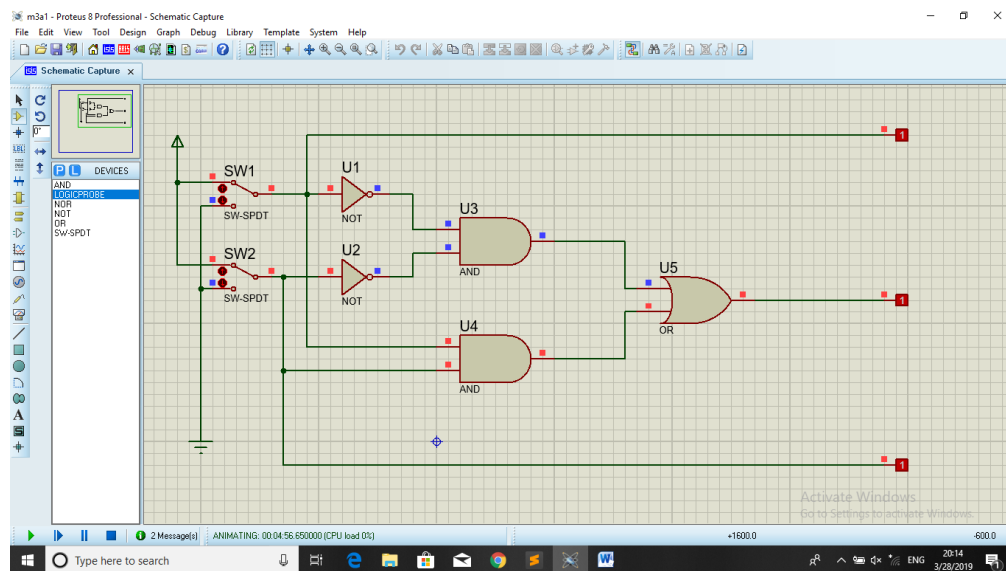


2. $L3 = \text{NOT}(L1L2) + L1 + L2 = \text{NOT}(L1 \text{ XOR } L2)$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	1
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

4. Time Diagram

 


5. Conclusion

The NOR gate in figure 4.5 form a logic from the **XNOR** gate.

5. Trial 5: Designing Boolean function to the circuit

1. Make the circuit

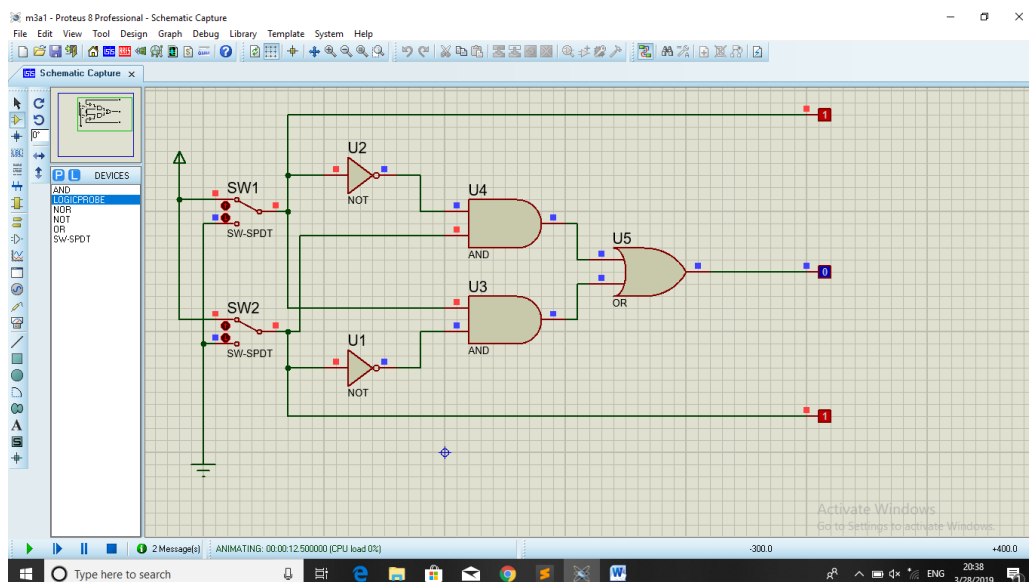


2. $L3 = \text{NOT}(L1) L2 + L1 \text{NOT}(L2)$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	0

4. Time Diagram

 

5. Conclusion

The NOR gate in figure 4.5 form a logic from the **XOR** gate.